



ConceptTest 26.2a

Parallel Resistors I

In the circuit below, what is the current through R_1 ?

- 1) 10 A
- 2) zero
- 3) 5 A
- 4) 2 A
- 5) 7 A

