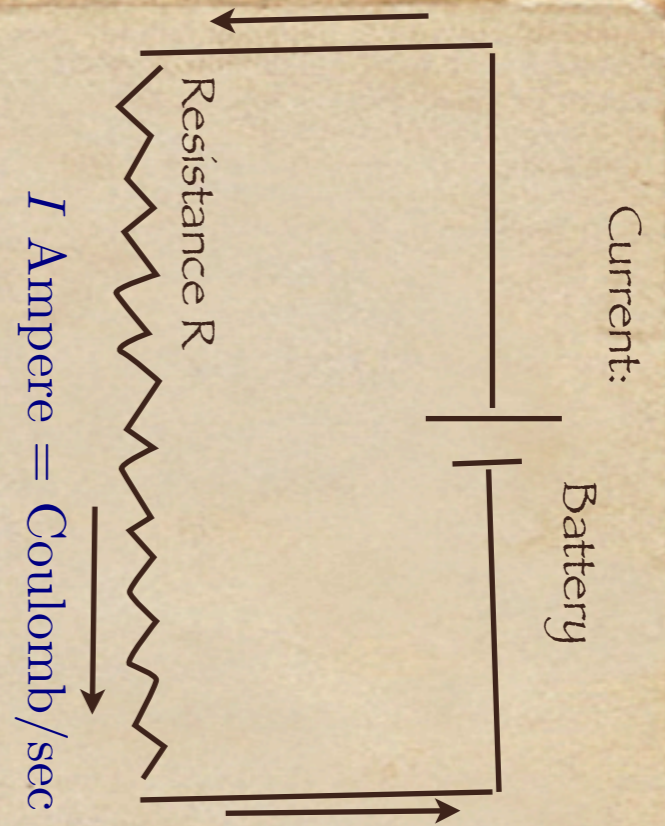


Lecture 14
May 2, 2012



Useful Analogy: Charge "Q" is the total quantity of water in a tank.


Current "I" is the amount of water flowing through a pipe per second

Unlike charge, the current has a direction. We may speak of Q as a scalar and I as a vector.

$$I = \frac{Q}{\Delta t}$$

Example1: 100 Coulombs in 10 seconds gives a current of 10 amperes

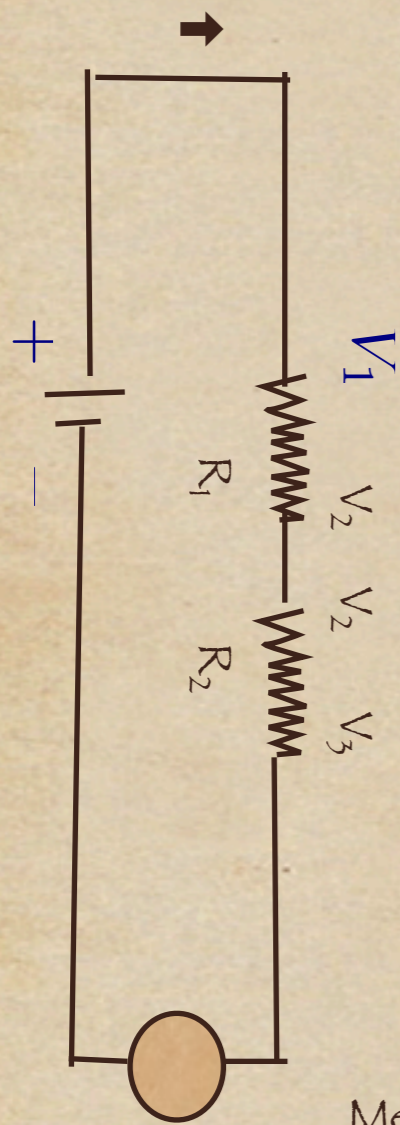Example2: A bulb has a flow of 1 amp and is used for 10 minutes. Total charge = 600 seconds x 1 ampere = 600 Coulombs



$V_1 - V_2$ is like $H_1 - H_2$

$V_2 - V_3$ is like $H_2 - H_3$

Battery voltage is the total potential drop

$V = V_1 - V_3$

Measures current (Ammeter)

Water flow in a terrace

Water	Electricity
Total water in tank	Charge Q in battery [Coulomb]
Rate of flow of water in a pipe	Current I [Amperes]
Height of tank	Potential V [Volts]
Height difference	Potential difference
Constriction of pipe carrying water	Resistance R [Ohms]
Work done in forcing water through a pipe	Work done in pushing charge through a
Rate of doing work is power {watts}	Rate of doing work is power P {watts}

Voltage = potential difference


W = work done in moving a charge against a potential

$$V = V_1 - V_2$$


$$W = V \times Q$$

$$[V] = \text{Joules/Coulomb}$$

$$[V] = \text{Volt}$$

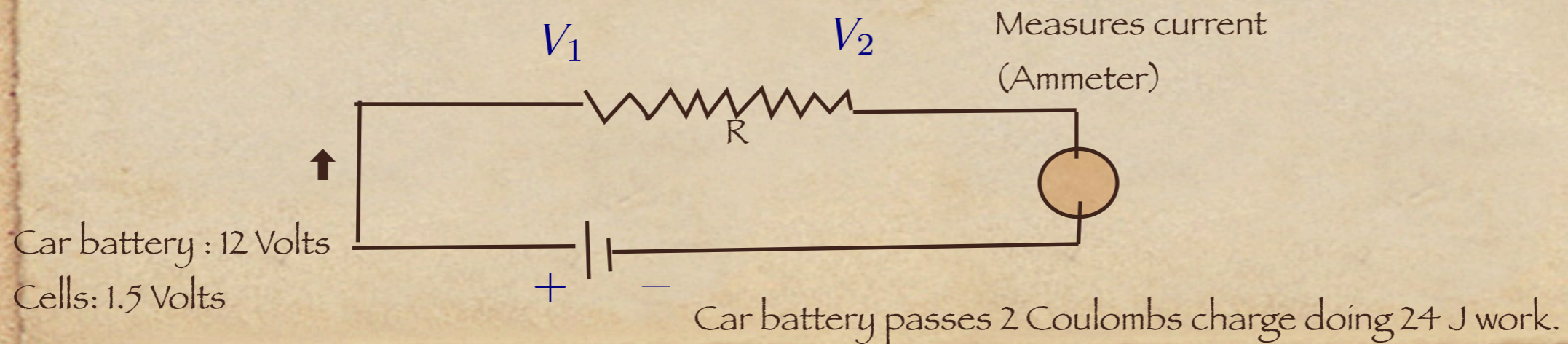

Resistance and Ohm's law

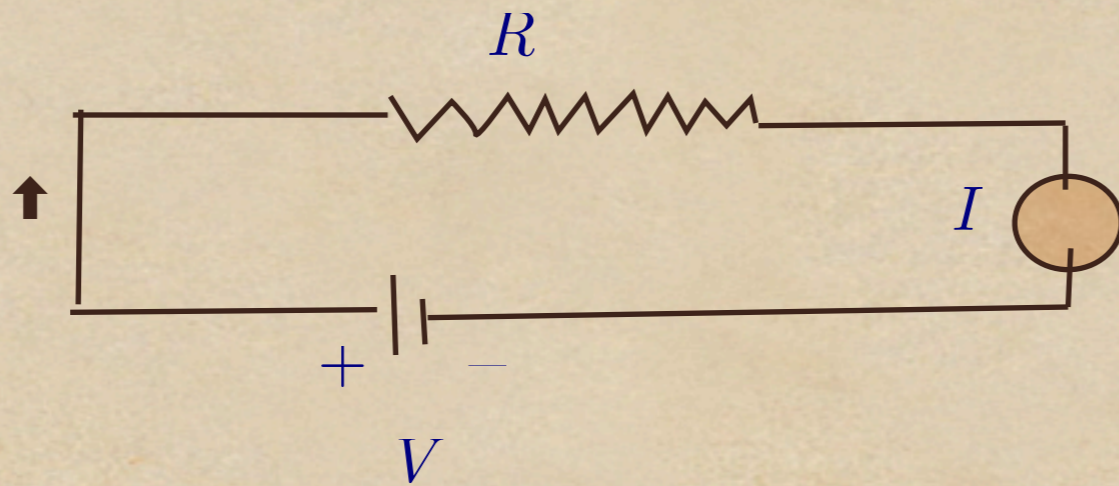

$$V = I \times R$$

$$R = \frac{V}{I}$$

$$[R] = \text{Ohms} \rightarrow \Omega$$

$$[R] = \text{Volts/Ampere}$$

True for most metallic wires

R = resistance of the wire

Example : Battery 12 V, connect to resistance 1 Ohm gives current of 12 ampere.

by changing the resistance, we change the current in this situation

Work done and power relationship

Summarizing:

A) we saw that a charge Q can be moved against a voltage V and the work done is $W = Q \times V$. Here Q is in Coulombs, V in volts, and W is in Joules (recall work done is dimensionally the same as energy).

B) We also saw that the current I is related to charge Q through $I = Q/\Delta t$ where the variable Δt is the time interval during which Q flows.

C) Now recall that power P is the rate of doing work, i.e.

$P = W/\Delta t$. Hence

$P = Q \times V / \Delta t$

We now use the definition of current above and conclude that

$P = V \times I$

Here if we write V in volts and I in Coulomb per second (i.e. amperes) then P is automatically in Watts.

Current, Voltage, and Power redux

$$I = f(V)$$



I Amperes

V Volts

$$P = I V \text{ Power in Watts}$$

$V = I \times R$ Ohm's Law for resistances (Linear curves)

$P = I^2 R$ for resistances

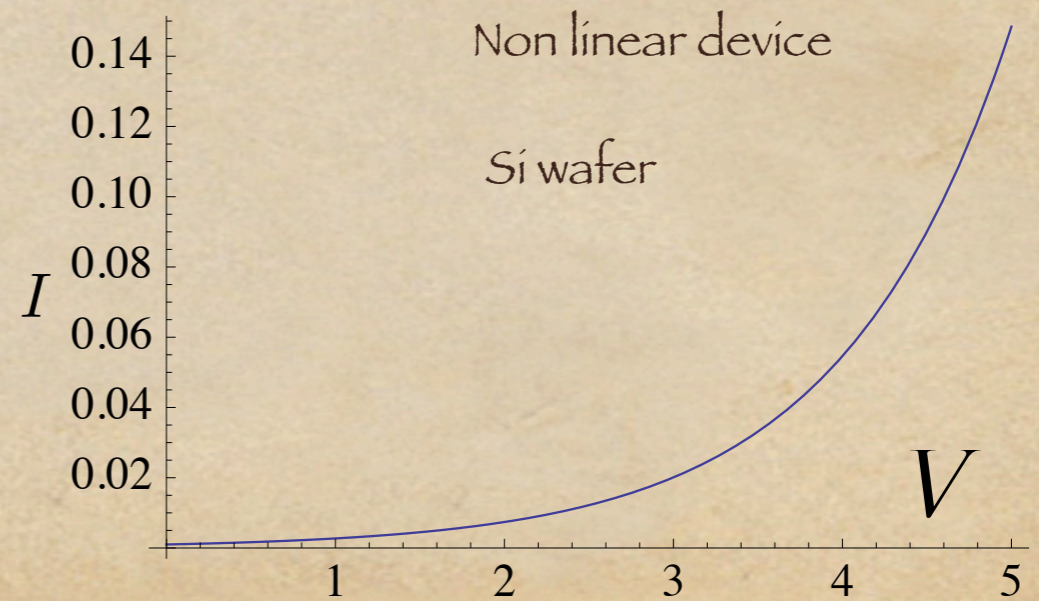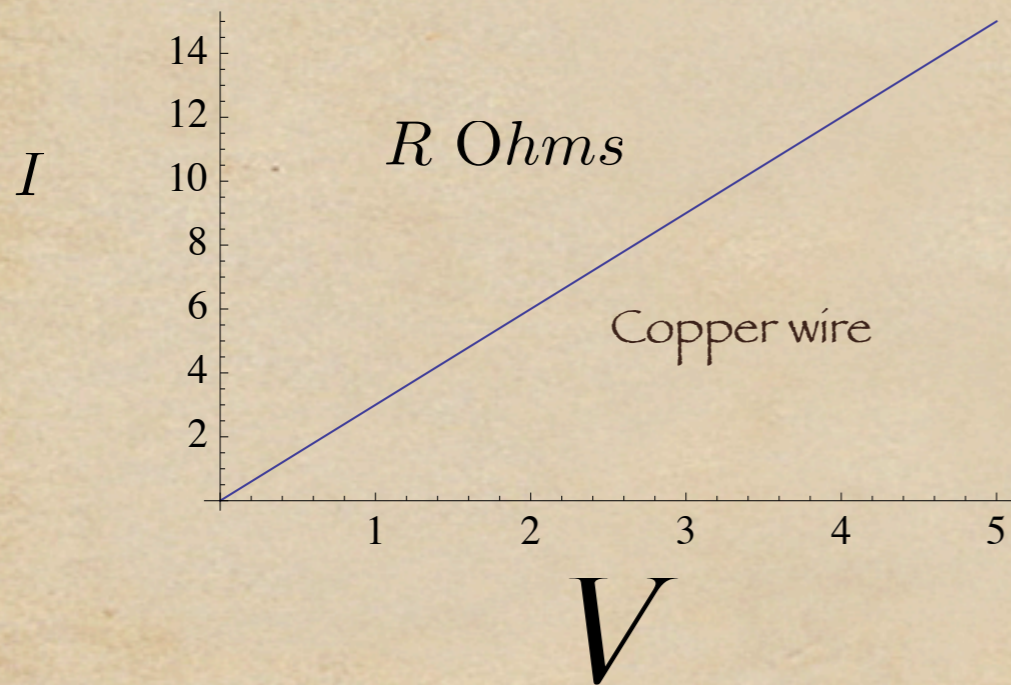

Now we do the quiz #2