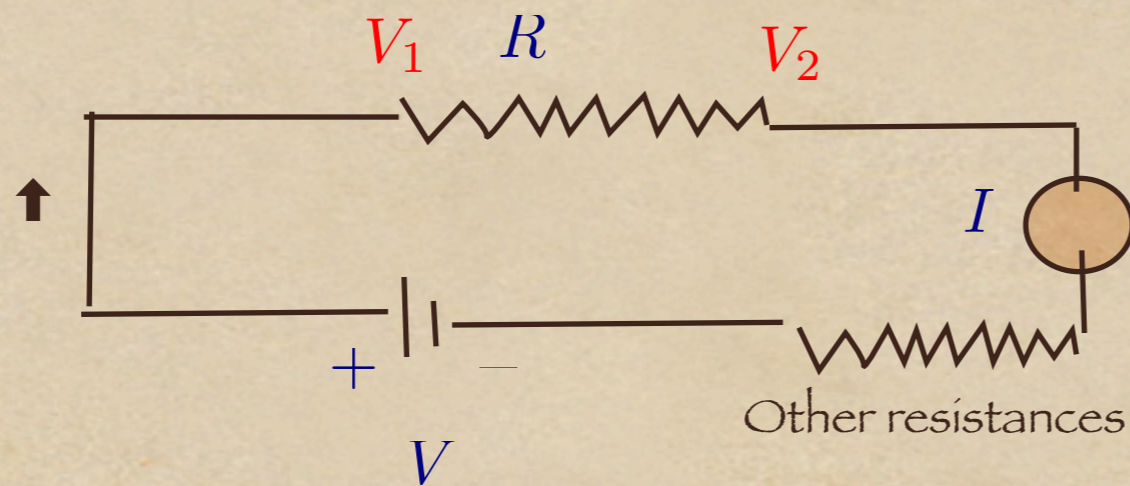


Lecture 15

May 4, 2012

Resistance and Ohm's law



$$[R] = \text{Ohms} \rightarrow \Omega$$

$V_1 - V_2 = I \times R$ Potential drop across R and current I are connected by Ohm's law

$P = (V_1 - V_2) \times I = I^2 \times R$ Power dissipated in (Joule) heating across R

Current, Voltage, and Power redux

$$V = I \times R \quad \text{Ohm's law}$$

$$I = f(V) \quad \text{More general than Ohm's law}$$



$V = I \times R$ Ohm's Law for resistances (Linear curves)

$P = I^2 R$ for resistances

V Volts

I Amperes

$P = I V$ Power in Watts

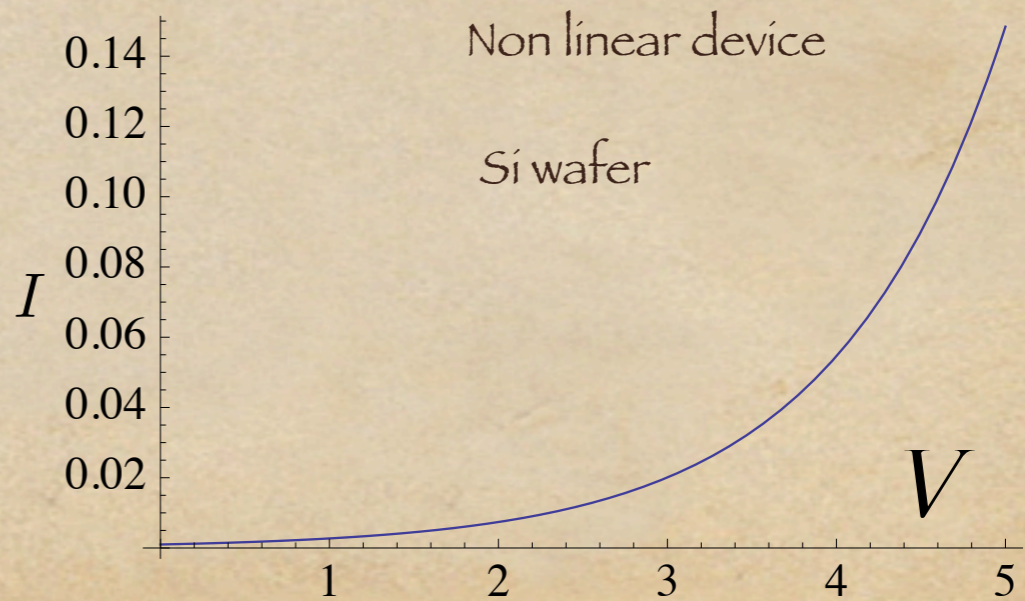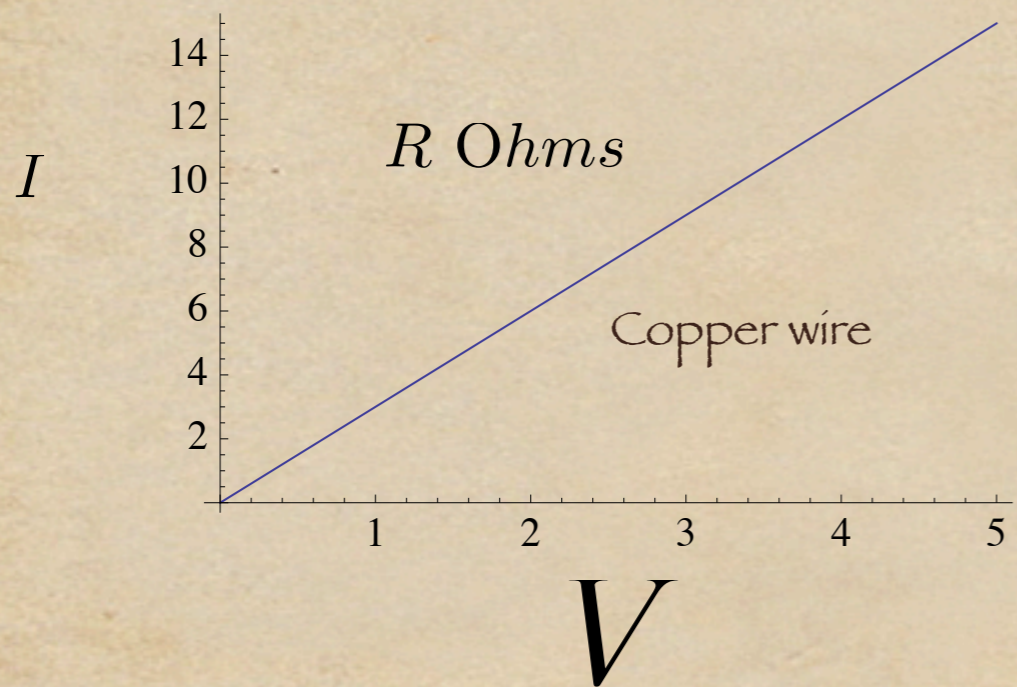


Household voltage 115 V (USA) 220 V (India) 240 V (UK)

DC = direct current
AC = alternating current

AC is much easier to generate using the idea of electromagnetic induction of Michael Faraday

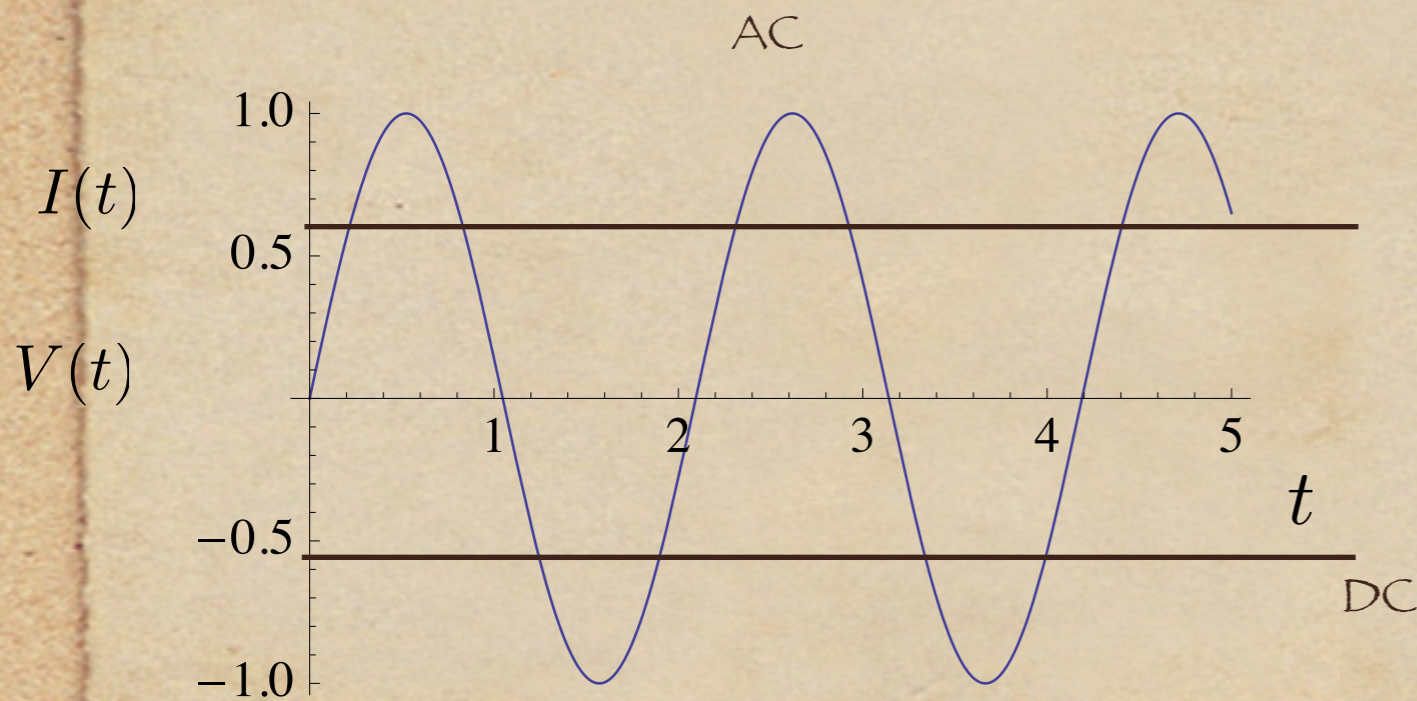Practical usage case: AC current and AC voltage, where these are time dependent



$$\sin(\omega t)$$

$$\omega = \frac{2\pi}{T}$$

Cycles per second
Household current
60 Hertz = 60 cycles per second

POWER and Energy used

$$P = I \times V \text{ Watts}$$

$$I \sim \text{Amps, \& } V \sim \text{Volts}$$

Joule Heating is covered in this equation

Example: 12 V battery drawing 10 amps current (high beam) consumes 120 Watts power

Combining Ohms law and Power equation, we can solve many problems.

$$V = I \times R \text{ (1)}$$

$$P = I \times V \text{ (2)}$$

P V R I

Four variables two equations
Hence given any two, the other two follow

1) Given Voltage Source

V

Connected to various resistances

R

$$I = V/R$$

$$P = V^2/R$$

11) Given Current Source

I

Connected to various resistances

R

$$V = IR$$

$$P = I^2 R$$

III) Given Voltage Source

V

Connected to various appliances with given

P

$$I = P/V$$

$$R = V^2/P$$

Question: Given 1000 Watts toaster running for 5 minutes, what is the current drawn and energy used, and charges to PG&E!!!

$$V = 115 \text{ Volts}$$

$$I = 1000/115 = 8.7 \text{ Amps}$$

$$R = V^2/P = 13.2 \text{ Ohms}$$

$$E = 1kW \times 5minutes \times 1 \text{ hour}/60minutes = .083kWH$$

$$\begin{aligned} &\times .12\$ \text{ per } kW H \\ &= .010\$ \end{aligned}$$

Cooking range	12 kW
Heat pump	12 kW
Clothes dryer	5 kW
Oven	3.2 kW
Microwave Oven	1.5 kW
Hand Iron	1 kW
Room Airconditioner	1.6 kW
TV	.33 kW

Determining Joule heating losses

We would like to be able to calculate the losses to Joule heat in various situations.

Suppose a 1000 MW power plant sends its power out on a 800,000 V high voltage line.

If the total resistance of the line is 2.2Ω , what percentage of the electrical power will be lost due to Joule heating?

We may find the current in the transmission line, because we know that $P = IV$, so $I = P/V$:

$$I = \frac{P}{V} = \frac{1000 \text{ MW}}{800\,000 \text{ V}} = \frac{1\,000\,000\,000 \text{ W}}{800\,000 \text{ V}} = 1250 \text{ A.}$$

The power in Joule heating is found by $P_{\text{Joule heating}} = I^2 R$,

$$P_{\text{Joule heating}} = I^2 R = (1250 \text{ A})^2 \times 2.2 \Omega = 3,437,500 \text{ W} = 3.44 \text{ MW.}$$

Hence $\frac{P_{\text{Joule heating}}}{P_{\text{transmitted}}} = \frac{3.44 \text{ MW}}{1000 \text{ MW}} = 0.344\%$ and so about one-third of a percent of the

transmitted electric power is lost to Joule heating in this case.

Question: What is the voltage at the end of the line?

We will return to this interesting question soon!

How about a lower voltage?

Same problem but now we transmit the power on a 400 Volt line

$$I = \frac{P}{V} = \frac{10^9 \text{ W}}{400\text{V}} = 2.5 \times 10^6 \text{ Amps}$$

Joule Heating:

$$P_{\text{Joule}} = I^2 \times R = 2.2 \times 6.25 \times 10^{12} = 1.37 \times 10^{13} \text{ W}$$

But !! $P_{\text{Generated}} = 10^9 \text{ W}$

This is a big problem!

$$P_{\text{Joule}} = I^2 \times R$$

$$P_{\text{Generated}} = I \times V$$

$$P_{\text{Joule}} = P_{\text{Generated}}^2 \times \frac{R}{V^2}$$

Big V is the solution.


Comment: In using the above relations, we should note that the Ohm's law needs to be handled carefully:

In particular we cannot use

$$V = I \times R \quad \text{Wrong formula}$$

to calculate I from the given line voltage V and resistance R .

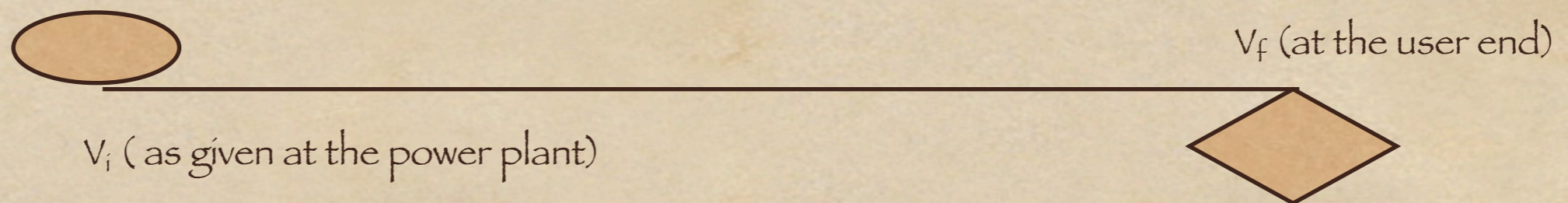Key point is that the voltage line has a potential drop across its length:



$$V_i - V_f = I \times R \quad \text{Correct formula}$$