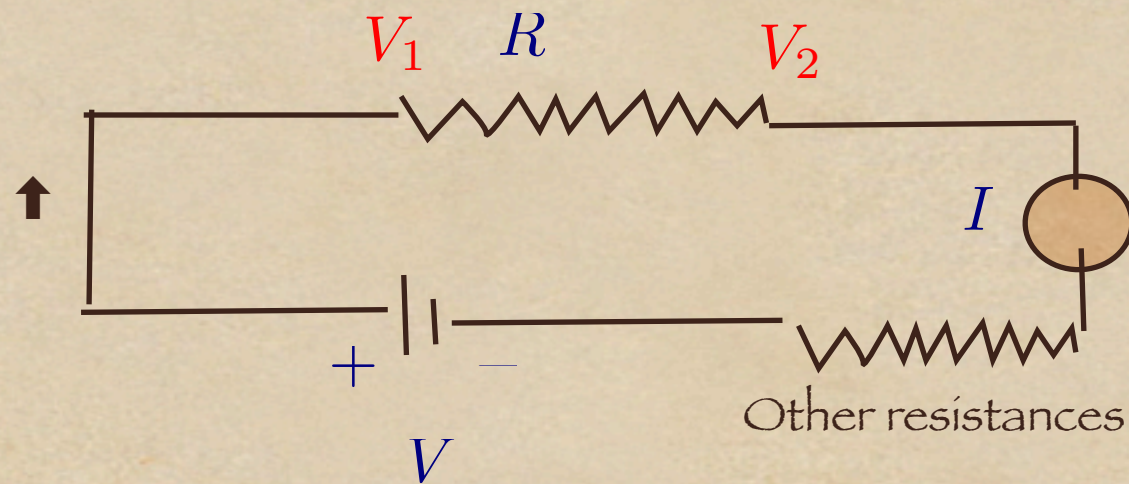


Lecture 16
May 9, 2012

Resistance and Ohm's law



$$[R] = \text{Ohms} \rightarrow \Omega$$

$V_1 - V_2 = I \times R$ Potential drop across R and current I are connected by Ohm's law


$P = (V_1 - V_2) \times I = I^2 \times R$ Power dissipated in (Joule) heating across R

For AC current we can use the same picture as before with battery replaced by V that stands for the power plant.

Now

R = transmission line resistance

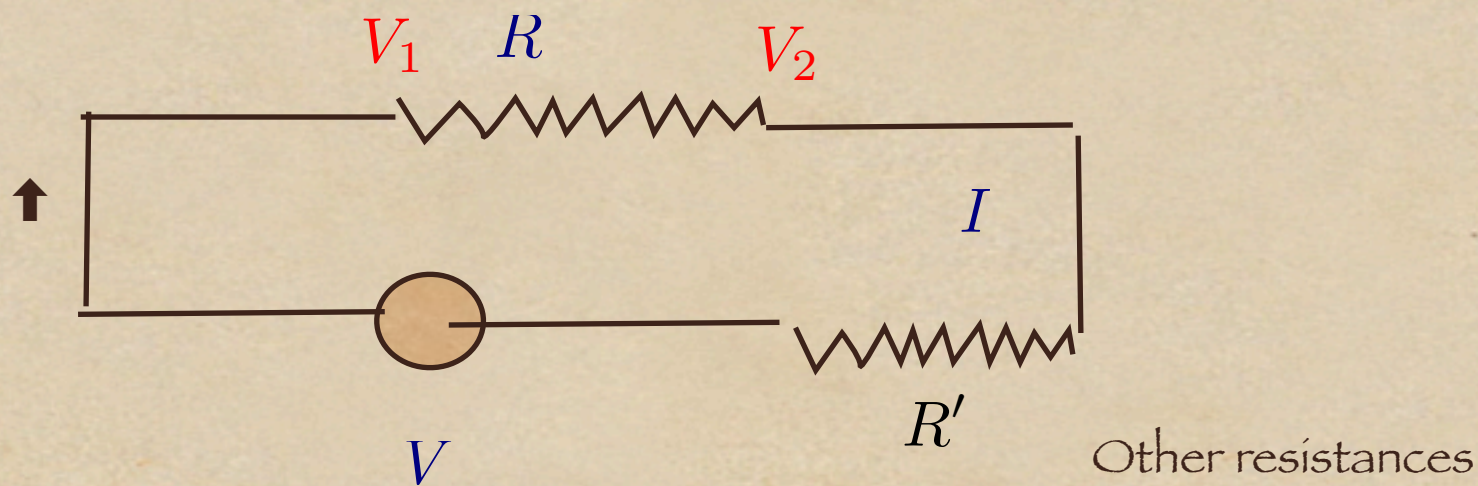R' = resistance of homes and communities ($R' \gg R$)



$V_1 - V_2 = I \times R$ Potential drop across R and current I are connected by Ohm's law


$P = (V_1 - V_2) \times I = I^2 \times R$ Power dissipated in (Joule) heating across R

$$I = V / (R' + R)$$

$$R' + R = R_{Total}$$

We next learn that this is an example of two resistances in **SERIES**

Resistors in "series"

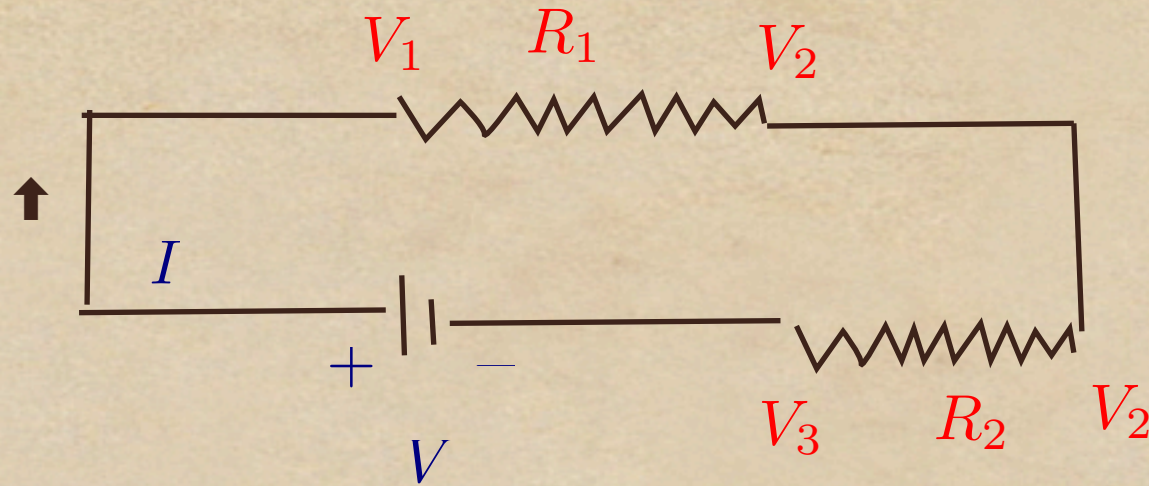

Note that the current I is common to both resistances.

$$V = V_1 - V_3, \quad (1)$$

$$V_1 - V_2 = I R_1, \quad (2)$$

$$V_2 - V_3 = I R_2, \quad (3)$$

Adding (2) and (3) we get on using (1)

$$V_1 - V_3 = V = I (R_1 + R_2), \quad (4)$$

Hence effective resistance is the sum of the two when placed in "series".

$$R_T = R_1 + R_2$$


$$V = I \times R_T$$

$$P_1 = (V_1 - V_2) \times I = I^2 R_1 = V^2 \frac{R_1}{R_T^2}, \quad (5)$$

Power dissipated in the resistor

$$P_2 = (V_2 - V_3) \times I = I^2 R_2 = V^2 \frac{R_2}{R_T^2}, \quad (6)$$

Resistors in "parallel"

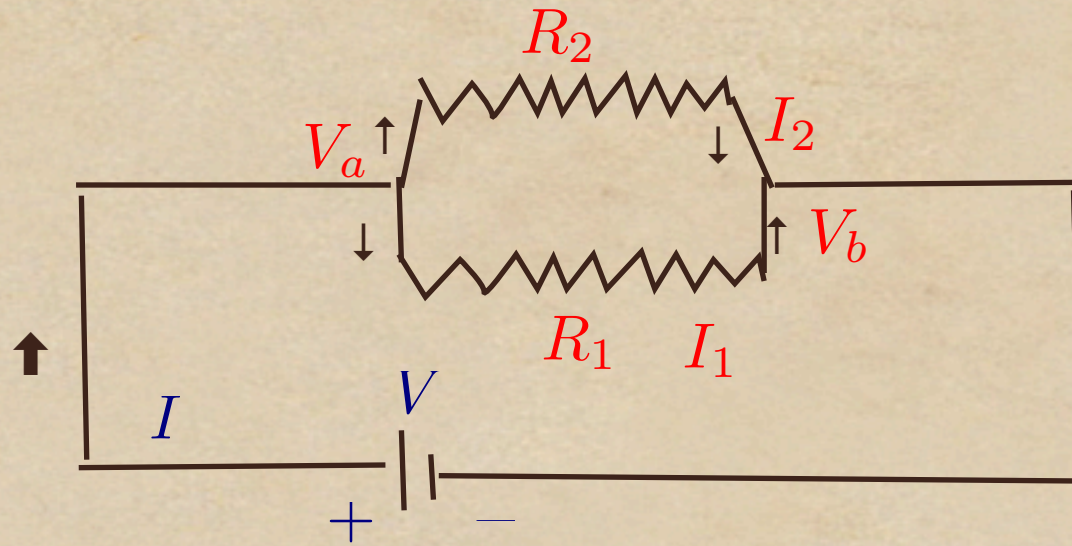

$$I = I_1 + I_2, \quad (1)$$

$$V = V_a - V_b, \quad (2)$$

$$V = I_1 \times R_1, \quad (3)$$

$$V = I_2 \times R_2, \quad (4)$$

Using (1) we write the total current as

$$I = V \times \left(\frac{1}{R_1} + \frac{1}{R_2} \right), \quad (5)$$

$$R_T = \frac{R_1 R_2}{R_1 + R_2}, \quad (6)$$

$$P_1 = V \times I_1 = \frac{V^2}{R_1}, \quad (7)$$

$$P_2 = V \times I_2 = \frac{V^2}{R_2}, \quad (8)$$

These 8 equations
give the complete solution

Numerical problem

Comparing the two

Series

Parallel

$$R_T = R_1 + R_2$$

$$R_T = \frac{R_1 R_2}{R_1 + R_2}, \quad (6)$$

$$P_1 = V^2 \frac{R_1}{R_T^2}, \quad \leftarrow \text{small}$$

$$\text{most of power used} \rightarrow P_1 = V \times I_1 = \frac{V^2}{R_1}, \quad (7)$$

$$P_2 = V^2 \frac{R_2}{R_T^2}, \quad \leftarrow \text{most of power used}$$

$$\text{small} \rightarrow P_2 = V \times I_2 = \frac{V^2}{R_2}, \quad (8)$$

If we take
 $R_1/R_2 = \text{very small}$