

Using Ohm's Law

Ohm's Law reads

$$V = IR.$$

If we know the current and the resistance, we may find the potential difference (voltage) between the ends of the piece of wire. For example, suppose a circuit element has a resistance of 50.0Ω and carries a current of 3.5 A (a). Then the potential difference between the ends of the piece of wire is

$$V = IR = (3.5 \text{ A}) \times (50.0 \Omega) = 175 \text{ V}.$$

A greater resistance would have led to a greater potential difference. If the resistance were 200Ω (b), the potential difference would have been

$$V = IR = (3.5 \text{ A}) \times (200.0 \Omega) = 700 \text{ V}.$$

A greater current for the same resistance would also have meant a greater potential difference. If $I = 10.0 \text{ A}$ (c), then the potential difference is

$$V = IR = (10.0 \text{ A}) \times (50.0 \Omega) = 500 \text{ V}.$$

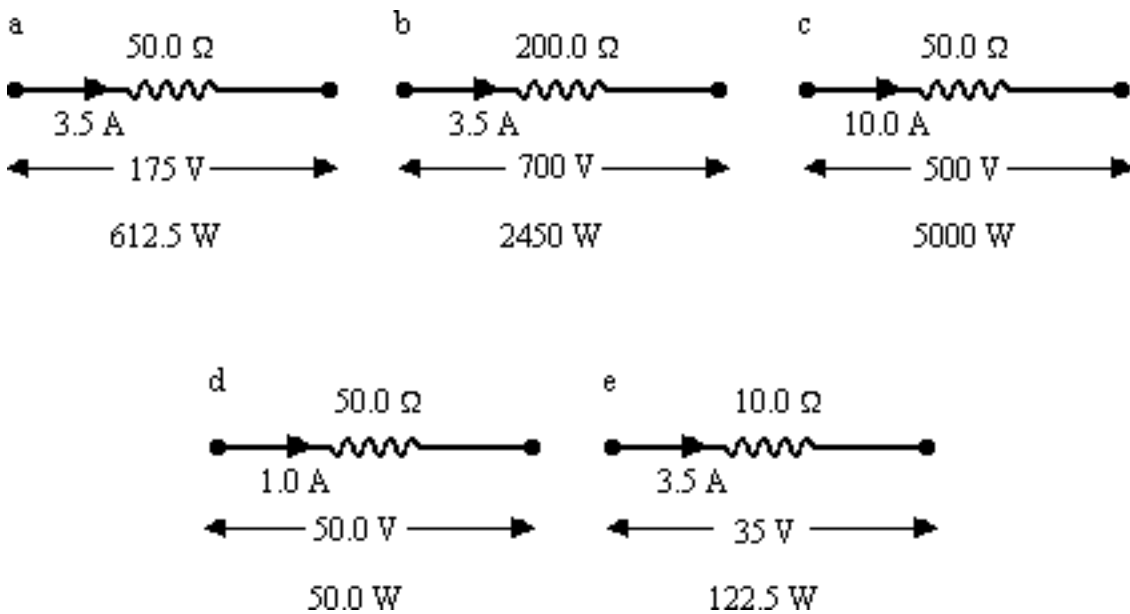


Fig. E04.3.1 Finding the voltage (potential difference) between ends of wires, and the amount of power dissipated. a. $I = 3.5 \text{ A}$, $R = 50.0 \Omega$ b. $I = 3.5 \text{ A}$, $R = 200.0 \Omega$ c. $I = 10.0 \text{ A}$, $R = 50.0 \Omega$ d. $I = 1.0 \text{ A}$, $R = 50.0 \Omega$ e. $I = 3.5 \text{ A}$, $R = 10.0 \Omega$

Similarly a smaller current, say $I = 1.0 \text{ A}$ (d), for the same resistance means a smaller potential difference

$$V = IR = (1.0 \text{ A}) \times (50.0 \text{ } \Omega) = 50.0 \text{ V}.$$

A smaller resistance $R = 10.0 \text{ } \Omega$, for the same current as in (a), 3.5 A (e) also means a smaller potential difference between the ends of the piece of wire,

$$V = IR = (3.5 \text{ A}) \times (10.0 \text{ } \Omega) = 35 \text{ V}.$$

Suppose we have a potential difference between two points of 100 V . If the current in the circuit element is 2.0 A , for example, we can determine the resistance to be

$$R = V/I = 100 \text{ V}/2.0 \text{ A} = 50.0 \text{ } \Omega.$$

A greater current flow will result if the resistance is smaller. For example, if the current in this circuit element having a potential difference of 100 V is 5.0 A , the resistance is lower:

$$R = V/I = 100 \text{ V}/5.0 \text{ A} = 20.0 \text{ } \Omega.$$

A smaller current flow will result when the resistance is greater. If the current in this same circuit element is 0.50 A , the resistance must have been

$$R = V/I = 100 \text{ V}/0.50 \text{ A} = 200.0 \text{ } \Omega.$$

Finally, if we know the potential difference between the ends of the piece of wire and the resistance, we can determine the current. Suppose a piece of wire has a potential difference between the ends of the wire of 100 V and has a resistance of $10.0 \text{ } \Omega$. The current is

$$I = V/R = 100 \text{ V}/10.0 \text{ } \Omega = 10.0 \text{ A}.$$

Just as above, we can see that increasing the potential difference for a given resistance means a greater current, and increasing the resistance for a given potential difference means a smaller current. The contrary also is true: decreasing the potential difference for a given resistance means a smaller current, and decreasing the resistance for a given potential difference means a greater current.

Finding power

We know that power is given as

$$P = IV.$$

If Ohm's Law, $V = IR$, is also true, then we may find the power simply. Let us use the examples from the first paragraph above. The power used in each situation is

$$P = IV = (175 \text{ V}) \times (3.5 \text{ A}) = 612.5 \text{ W};$$

$$P = IV = (700 \text{ V}) \times (3.5 \text{ A}) = 2450 \text{ W};$$

$$P = IV = (500 \text{ V}) \times (10.0 \text{ A}) = 5000 \text{ W};$$

$$P = IV = (50.0 \text{ V}) \times (1.0 \text{ A}) = 50.0 \text{ W}; \text{ and}$$

$$P = IV = (35 \text{ V}) \times (3.5 \text{ A}) = 122.5 \text{ W}, \text{ respectively}$$

If we know P and V we may determine I . Suppose in a circuit element that $V = 120 \text{ V}$ and $P = 1200 \text{ W}$. Then

$$I = P/V = 1200 \text{ W}/120 \text{ V} = 10 \text{ A}.$$

We may now use Ohm's Law to determine the resistance of the circuit element:

$$R = V/I = 120 \text{ V}/10 \text{ A} = 12 \Omega.$$

It is obvious in this case that if R had been known, the Joule heating relation $P = I^2R$ could have been used to determine I as

$$I = \sqrt{P/R} = \sqrt{1200 \text{ W}/12 \Omega} = \sqrt{100 \text{ A}^2} = 10 \text{ A}.$$

As another example, consider a 10 W flashlight bulb. The two batteries that operate it produce a potential difference of 3.0 V. A current of

$$I = P/V = 10 \text{ W}/3.0 \text{ V} = 3.33 \text{ A}.$$

will flow, the resistance may be found as

$$R = V/I = 3.0 \text{ V}/3.33 \text{ A} = 0.90 \Omega.$$

Note that the Joule heat equation is consistent:

$$P = I^2R = (3.33 \text{ A})^2 \times (0.90 \Omega) = 10 \text{ W}.$$

Determining Joule heating losses

We would like to be able to calculate the losses to Joule heat in various situations.

Suppose a 1000 MW power plant sends its power out on a 800,000 V high voltage line. If the total resistance of the line is 2.2 Ω , what percentage of the electrical power will be lost due to Joule heating?

We may find the current in the transmission line, because we know that $P = IV$, so $I = P/V$:

$$I = \frac{P}{V} = \frac{1000 \text{ MW}}{800\,000 \text{ V}} = \frac{1\,000\,000\,000 \text{ W}}{800\,000 \text{ V}} = 1250 \text{ A.}$$

The power in Joule heating is found by $P_{\text{Joule heating}} = I^2 R$,

$$P_{\text{Joule heating}} = I^2 R = (1250 \text{ A})^2 \times 2.2 \Omega = 3,437,500 \text{ W} = 3.44 \text{ MW.}$$

Hence $\frac{P_{\text{Joule heating}}}{P_{\text{transmitted}}} = \frac{3.44 \text{ MW}}{1000 \text{ MW}} = 0.344\%$ and so about one-third of a percent of the

transmitted electric power is lost to Joule heating in this case.

Let's do a similar example. Suppose a 750 MW power plant sends its power out on a 364,960 V high voltage transmission line. If 1 percent of the power is lost due to Joule heating on a section of transmission line, what is the resistance of the section?

Clearly, 1% of 750 MW is 7.5 MW, so 7.5 MW of power is dissipated as Joule heat. We know the current in the line because, as mentioned above, $I = P/V$, where P is the power produced at the plant and V is the transmission line voltage. Then the current in the transmission line is

$$I = P/V = \frac{750\,000\,000 \text{ W}}{364\,960 \text{ V}} = 2055 \text{ A,}$$

and the Joule heat dissipated is $P_{\text{Joule heating}} = I^2 R$,

$$P_{\text{Joule heating}} = 7.5 \text{ MW} = (2055 \text{ A})^2 R,$$

so we may write

$$R = \frac{7\,500\,000\text{ W}}{4\,223\,025\text{ A}^2} = 1.78\text{ W/A}^2 = 1.78\text{ V/A} = 1.78\ \Omega.$$

This transmission line has a resistance of $1.78\ \Omega$.

In our final examples, a 600 MW power plant sends its power out on a high voltage line. If the total resistance of a section of the line is $160\ \Omega$, and 5% of the power is lost due to Joule heating, what is the voltage of the transmission line? We first find the loss to Joule heat, $P_{\text{Joule heating}} = (0.05) \times (600\text{ MW}) = 30\text{ MW}$. We know that $P_{\text{Joule heating}} = I^2 R$, so we may determine the current in the transmission line from

$$I^2 = \frac{30\,000\,000\text{ W}}{160\ \Omega} = 187,500\text{ A}^2.$$

Taking the square root of this number, we find a current if $I = 433\text{ A}$. Since the power coming from the power plant is $P = IV$, the voltage of the transmission line must be

$$V = \frac{P}{I} = \frac{600\,000\,000\text{ W}}{433\text{ A}} = 1,385,681\text{ V}.$$

This is not a realistic problem because there are no transmission lines operating with such high voltage. The 765,000 V transmission lines are the highest voltage lines currently in use. What if the 600 MW transmission line had a Joule heating loss of 30 MW at a voltage of 765,000 V? What would the line's resistance have to be? As in the example of the 750 MW power plant, we have

$$I = P/V = \frac{600\,000\,000\text{ W}}{765\,000\text{ V}} = 784.3\text{ A},$$

so $I^2 = 615,148\text{ A}^2$ and

$$R = \frac{30\,000\,000\text{ W}}{615\,148\text{ A}^2} = 48.77\text{ W/A}^2 \approx 48.8\text{ V/A} = 48.8\ \Omega.$$